



Studentsgroup:		Responsible for lab report:
Date:		Other participants
Lecturer:		

**Task 2:**

## Diode

### 1. Forward characteristics of a silicon and germanium diode

Use an XY-plotter to plot the forward IV-characteristics  $I_F = f(U_F)$  of a germanium diode AA138 and a silicon diode 1N4148 for forward currents in the range of  $I_F = 0..10\text{mA}$ .

**Post processing:**

- a) Using the measured IV-characteristic plot, determine the differential (small-signal) resistance for both diodes at  $I_F = 2\text{mA}$ .


### 2. Forward characteristic of the Silicon diode

Measure the forward voltage of the silicon diode 1N4148 for forward currents in the range of  $10\mu\text{A} \dots 100\text{mA}$ . Measure 3 points per each current decade. For example  $10\mu\text{A}$ ,  $20\mu\text{A}$ ,  $50\mu\text{A}$ ,  $100\mu\text{A}$ ,  $200\mu\text{A}$ , ....

**Post processing:**

- a) Plot the IV characteristics graphically using MATLAB or MS Excel. The y-axis ( $I_F$ ) should be plotted logarithmically.

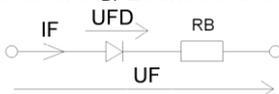
- b) Assume that the diode can be modelled by a series connection of Shockley diode  $I_F = I_S \cdot e^{\frac{U_{FD}}{m \cdot U_T}}$  and a resistor  $R_B$ . Estimate the diode parameters  $I_S$ ,  $m$  und  $R_B$ .



- c) Plot the diode characteristic using the parameters obtained in b) and compare the IV-characteristics graph with the measurement plot in a).
- d) Calculate the differential (small-signal) resistance of the diode using the Shockley equation at  $I_F = 2\text{mA}$  with the parameters obtained in 1a).
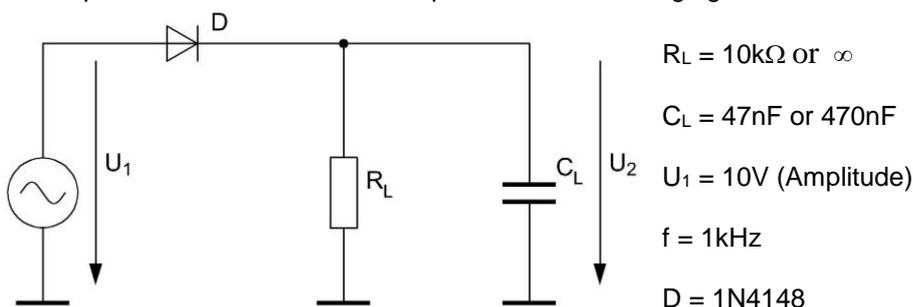
### 3. Half-wave rectifier/peak detector

Set up the half-wave rectifier as depicted in the following figure:



3.1 Use an oscilloscope to plot the time varying input and output signals ( $U_1$  and  $U_2$ ) versus time for  $C_L = 470\text{nF}$ , and  $R_L = \infty$ . Export and save the plots as graphical data.

3.2 Use an oscilloscope to plot the time varying input and output signals ( $U_1$  and  $U_2$ ) versus time for both cases  $C_L = 47\text{nF}$  und  $470\text{nF}$  simultaneously ( $R_L = 10\text{k}\Omega$ ). Determine the period of  $U_1$  and  $U_2$ . Export and save the plots as graphical data.


3.3 Use a METHRAHIT digital millimeter to measure the total effective value, the AC-effective value (the effective value of the ripple) and the average value of  $U_1$  and  $U_2$  for both cases  $C_L = 47\text{nF}$  und  $470\text{nF}$  ( $R_L = 10\text{k}\Omega$ ).

#### Post processing:

a) Calculate the *ripple factor* which is defined as the ratio of the effective value of the ripple voltage to the average value of  $U_2$ .
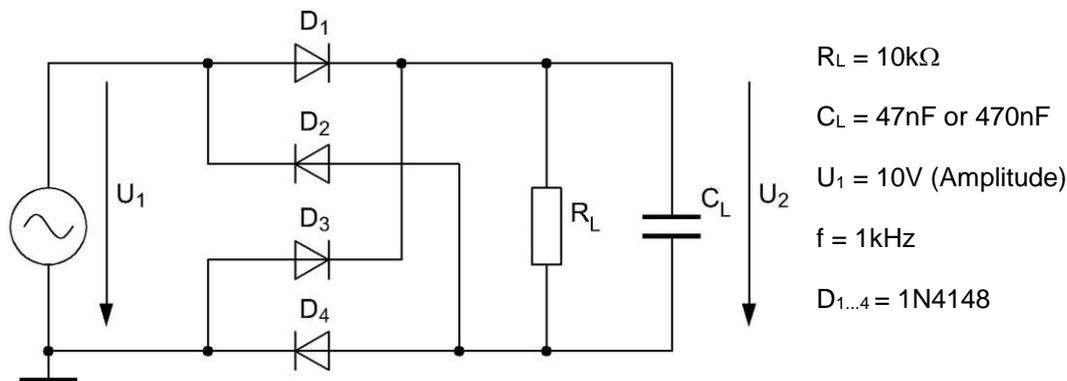
#### 4. Full-wave rectifier

Set up the half-wave rectifier as depicted in the following figure



4.1 Use an oscilloscope to plot the time varying input and output signals ( $U_1$  and  $U_2$ ) versus time for both cases  $C_L = 47\text{nF}$  und  $470\text{nF}$  simultaneously. Export and save the plots as graphical data. Determine the period of  $U_1$  and  $U_2$ .

**Hint:** A normal probe measures the potential difference between the probed signal with respect to ground node potential which is common to both probes 1 & 2 of the oscilloscope. Therefore,  $U_2$  cannot be measured using a normal oscilloscope probe. For this measurement you should use the *differential probe* which is available in the lab and measures the difference between two arbitrary potentials.

4.2 Use a METHRAHIT digital millimeter to measure the total effective value, the AC-effective value (the effective value of the ripple) and the average value of  $U_1$  and  $U_2$  for both cases  $C_L = 47\text{nF}$  und  $470\text{nF}$ .

#### Post processing:

a) Calculate the ripple factor which is defined as the ratio of the effective value of the ripple voltage to the average value for  $U_2$ . Compare the result with the results from 3a).